

Part 2

1 General Consideration of Negative Feedback Amplifiers

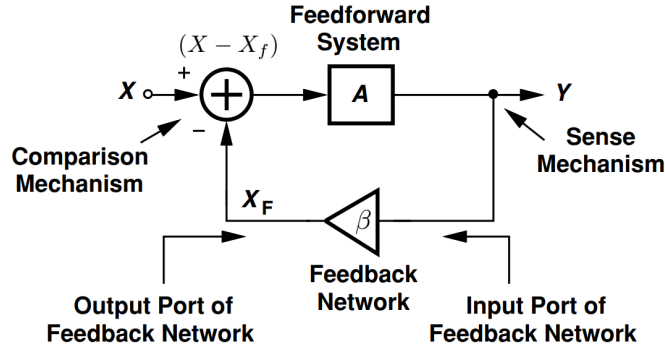


Figure 1

$$A_f = \frac{Y}{X} = \frac{A}{1 + \beta A} \quad (1)$$

A_f : Closed loop gain.

A : Open loop gain.

β : Feedback factor.

βA : Loop gain.

2 Characteristics of Feedback Amplifier

2.1 Gain Desensitivity

(A) Special case : if $\beta A \gg 1$

$$A_f = \frac{A}{1 + \beta A} \approx \frac{1}{\beta}$$

A_f in this case doesn't depend on A

(B) General case:

$$\begin{aligned} A_f &= \frac{1}{1 + \beta A} \\ \frac{dA_f}{dA} &= \frac{1}{(1 + \beta A)^2} < 1 \\ \frac{dA_f}{A_f} &= \frac{1}{1 + \beta A} \frac{dA}{A} \\ \therefore \frac{dA_f}{A_f} &< \frac{dA}{A} \end{aligned}$$

2.2 Bandwidth Extension

$$\text{Closed Loop Gain} = \frac{A_0}{1 + \beta A}$$

$$\text{Closed Loop Bandwidth} = (1 + \beta A)\omega_0$$

In other words, the gain and bandwidth are scaled by the same factor but in opposite directions, displaying a *constant* product.

	DC-gain	3 dB BW
Feedforward Amp. $A(s)$	A_0	ω_0
Feedback Amp. $A_f(s)$	$\frac{A_0}{1 + \beta A}$	$(1 + \beta A)\omega_0$

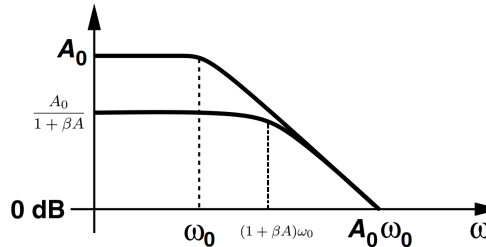


Figure 2

2.3 Linearity Improvement

A system placed in a negative feedback loop provides a more uniform gain for different signal levels.

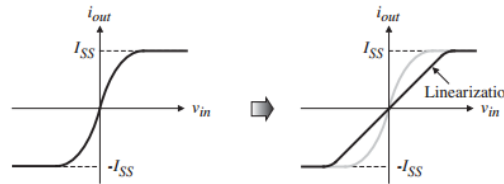


Figure 3

(3) 2.4 Effect on Noise

If noise N is added to the signal X

$$Y = \frac{A}{1 + \beta A} X + \frac{A}{1 + \beta A} N$$

$$\text{SNR}_i = \text{SNR}_o = \frac{X}{N} \quad (6)$$

(4) Negative feedback amplifier reduces the gain inside the loop. However, it doesn't change the SNR.

(5) 3 Types of Amplifiers

Input	Output	Type	Gain
V	V	Voltage amplifier	$A_v \frac{V}{V}$
I	V	Transresistance amplifier	$R_m \frac{V}{A}$
V	I	Transconductance amplifier	$G_m \frac{A}{V}$
I	I	Current amplifier	$A_i \frac{A}{A}$

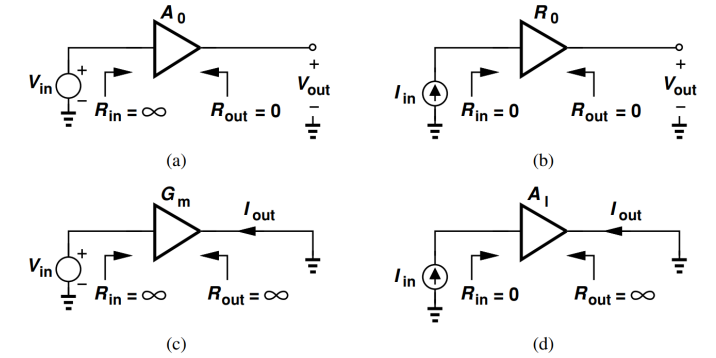


Figure 4: (a) Voltage, (b) transresistance, (c) transconductance, and (d) current amplifiers.

3.1 Voltage Amplifier

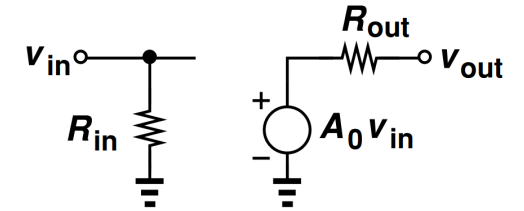


Figure 5

Voltage gain :

$$A_v = \left. \frac{V_o}{V_i} \right|_{R_L=\infty}$$

Input resistance:

$$R_i = \frac{V_i}{I_i} \rightarrow \infty \text{ (ideal)}$$

Output resistance:

$$R_o = \left. \frac{V_o}{I_o} \right|_{V_i=0} \rightarrow 0 \text{ (ideal)}$$

3.2 Transresistance Amplifier

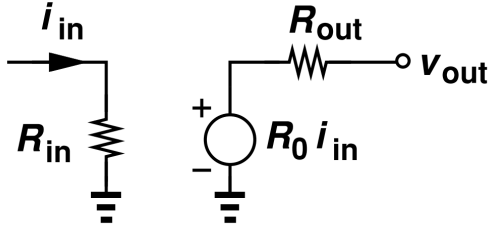


Figure 6

Voltage gain :

$$R_m = \left. \frac{V_o}{I_i} \right|_{R_L=\infty}$$

Input resistance:

$$R_i = \frac{V_i}{I_i} \rightarrow 0 \text{ (ideal)}$$

Output resistance:

$$R_o = \left. \frac{V_o}{I_o} \right|_{I_i=0} \rightarrow 0 \text{ (ideal)}$$

3.3 Transconductance Amplifier

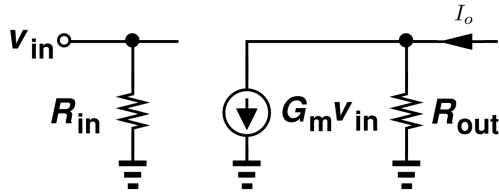


Figure 7

Voltage gain :

(7)

$$G_m = \left. \frac{I_o}{V_i} \right|_{R_L=0}$$

Input resistance:

(8)

$$R_i = \frac{V_i}{I_i} \rightarrow \infty \text{ (ideal)}$$

Output resistance:

(9)

$$R_o = \left. \frac{V_o}{I_o} \right|_{V_i=0} \rightarrow \infty \text{ (ideal)}$$

3.4 Current Amplifier

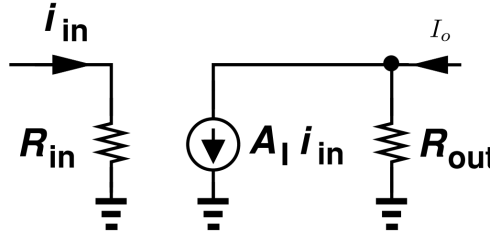


Figure 8

Voltage gain :

(10)

$$A_i = \left. \frac{I_o}{I_i} \right|_{R_L=0}$$

(11)

Input resistance:

(12)

Output resistance:

$$R_o = \left. \frac{V_o}{I_o} \right|_{I_i=0} \rightarrow \infty \text{ (ideal)}$$

4 Sensing and Returning Techniques



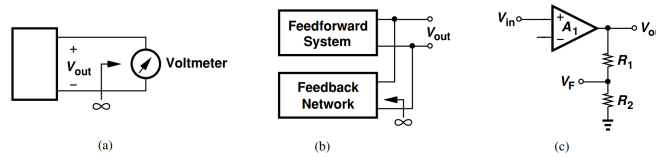


Figure 9: (a) Sensing a voltage by a voltmeter, (b) sensing the output voltage by the feedback network, (d) example of implementation.

(13)

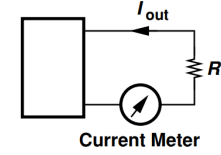

(14)

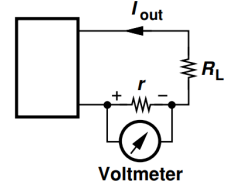

(15)


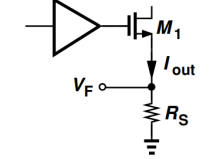
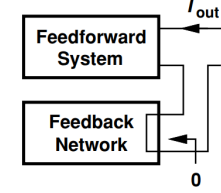


Figure 10: (a) Sensing a current by a current meter, (b) actual realization of current meter, (c) sensing the output current by the feedback network, (d) example of implementation.

(16)

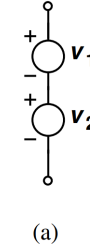

(17)

(a)


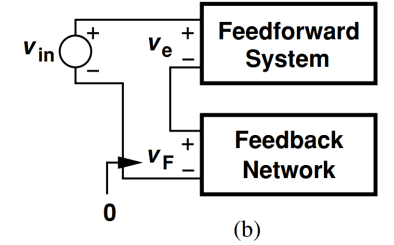



Figure 11: (a) Addition of two voltages, (b) addition of feedback and input voltages.

(18)

$$R_o = \left. \frac{V_o}{I_o} \right|_{I_i=0} \rightarrow \infty \text{ (ideal)}$$

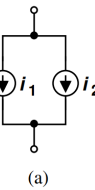

(a)

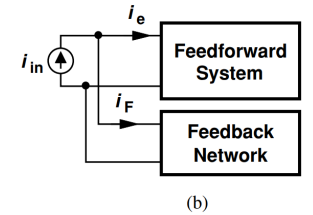

(b)

Figure 12: (a) Addition of two currents, (b) addition of feedback current and input current.

5 Feedback Topology

5.1 Voltage Voltage Feedback

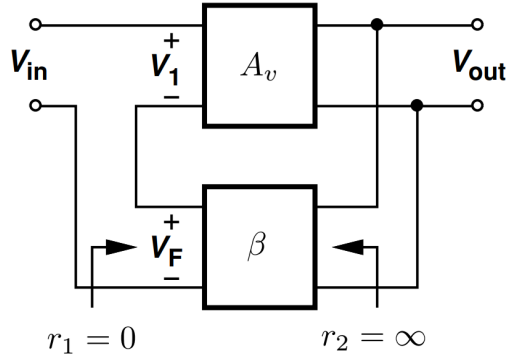


Figure 13

Closed loop gain:

$$A_{vf} = \frac{A_v}{1 + \beta A_v}$$

Input impedance:

$$R_{if} = R_i(1 + \beta A_v)$$

Input impedance is enhanced (closer to the ideal case (∞))

Output impedance:

$$R_{of} = \frac{R_o}{1 + \beta A_v}$$

Output impedance is enhanced (closer to the ideal case (0))

5.2 Voltage Current Feedback

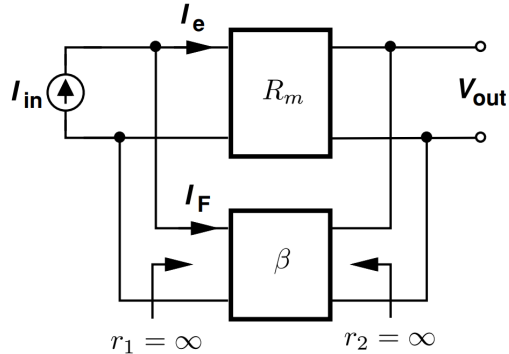


Figure 14

Closed loop gain:

$$R_{mf} = \frac{R_m}{1 + \beta R_m} \quad (22)$$

Input impedance:

$$R_{if} = \frac{R_i}{1 + \beta R_m} \quad (23)$$

Input impedance is enhanced (closer to the ideal case (0))

Output impedance:

$$R_{of} = \frac{R_o}{1 + \beta R_m} \quad (24)$$

Output impedance is enhanced (closer to the ideal case (0))

5.3 Current Voltage Feedback

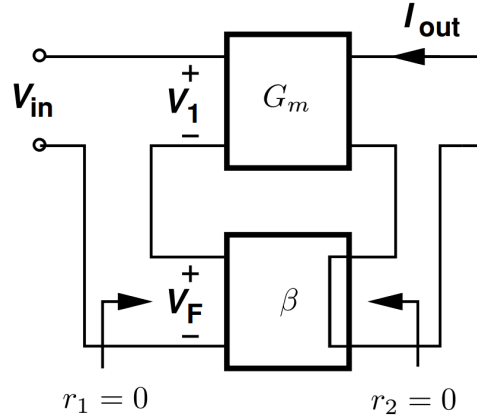


Figure 15

Closed loop gain:

$$G_{mf} = \frac{G_m}{1 + \beta G_m} \quad (25)$$

Input impedance:

$$R_{if} = R_i(1 + \beta G_m) \quad (26)$$

Input impedance is enhanced (closer to the ideal case (∞))

Output impedance:

$$R_{of} = R_o(1 + \beta G_m) \quad (27)$$

Output impedance is enhanced (closer to the ideal case (∞))

5.4 Current Current Feedback

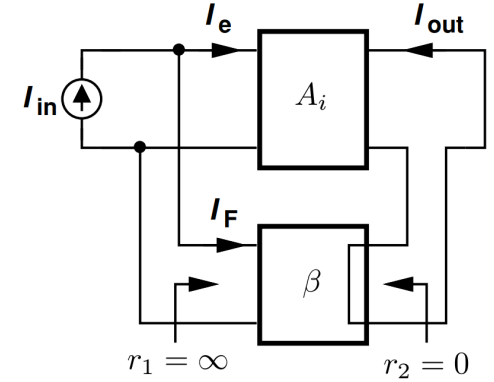


Figure 16

Closed loop gain:

$$A_{if} = \frac{A_i}{1 + \beta A_i} \quad (28)$$

Input impedance:

$$R_{if} = \frac{R_i}{1 + \beta A_i} \quad (29)$$

Input impedance is enhanced (closer to the ideal case (0))

Output impedance:

$$R_{of} = R_o(1 + \beta A_i) \quad (30)$$

Output impedance is enhanced (closer to the ideal case (∞))

6 Amplifier Frequency Response

7 Amplifier Gain

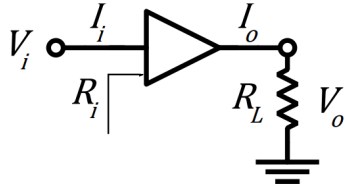


Figure 17

7.1 Gain as Ratio

Voltage Gain:

$$A_v = \frac{V_o}{V_i} \quad (31)$$

Current Gain:

$$A_i = \frac{I_o}{I_i} \quad (32)$$

Power Gain:

$$A_p = \frac{P_o}{P_i} = \frac{V_o I_o}{V_i I_i} = A_v \times A_i$$

If $R_i = R_L$:

$$A_p = A_v^2 = A_i^2 \quad (34)$$

7.2 Gain in Decibel

Power gain in (dB):

$$A_{p, \text{dB}} = 10 \log_{10}(A_p) \quad (\text{dB}) \quad (35)$$

Voltage gain in (dB):

$$A_{v, \text{dB}} = 20 \log_{10}(A_v) \quad (\text{dB}) \quad (36)$$

Current gain in (dB):

$$A_{i, \text{dB}} = 20 \log_{10}(A_i) \quad (\text{dB}) \quad (37)$$

In cascaded amplifiers:

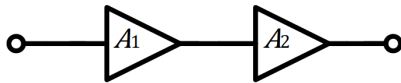


Figure 18

$$A_{\text{total}} = A_1 \times A_2 \quad (38)$$

$$A_{\text{total, dB}} = A_{1, \text{dB}} + A_{2, \text{dB}}$$

- When A_p **increases** by (3dB), it means it is **multiplied** by 2

- When A_p **decreases** by (3dB), it means it is **divided** by 2

- When A_v **increases** by (3dB), it means it is **multiplied** by $\sqrt{2}$
- When A_v **decreases** by (3dB), it means it is **divided** by $\sqrt{2}$

- When A_i **increases** by (3dB), it means it is **multiplied** by $\sqrt{2}$
- When A_i **decreases** by (3dB), it means it is **divided** by $\sqrt{2}$

8 dBm Power Measurement

$$P_{\text{dBm}} = 10 \log_{10} \left(\frac{P(\text{mW})}{1(\text{mW})} \right) \quad (\text{dBm}) \quad (39)$$

$$P_{\text{dB}\mu} = 10 \log_{10} \left(\frac{P(\text{mW})}{1(\mu\text{W})} \right) \quad (\text{dB}\mu) \quad (40)$$

9 Frequency Response

$$H(j\omega) = A(\omega)e^{j\phi(\omega)} \quad (41)$$

$A(\omega)$: Magnitude response.

$\phi(\omega)$: phase response.

$$Y(j\omega) = H(j\omega)X(j\omega) \quad (42)$$

$Y(j\omega)$: Output signal.

$H(j\omega)$: Frequency response.

$X(j\omega)$: Input signal.

10 Transfer Function

Notice that Fourier transform does not exist for many signals of interest.

For a wider class of signals, Laplace transform can be used by replace each $j\omega$ by $s = \sigma + j\omega$

$$H(s) = A(s)e^{\phi(s)} \quad (43)$$

$$Y(s) = H(s)X(s) \quad (44)$$

Transfer function in fraction form :

$$H(s) = K \frac{(s - s_{z1})(s - s_{z2}) \cdots (s - s_{zM})}{(s - s_{p1})(s - s_{p2}) \cdots (s - s_{pN})} = K \frac{\Pi_m(s - s_{zm})}{\Pi_n(s - s_{pn})} \quad (45)$$

11 Relation Between Frequency Response and Transfer Function

$$H(j\omega) = H(s)|_{s=0+j\omega} \quad (46)$$

12 Bode Plot: Real Zeros and Poles

Transfer function:

$$H(s) = K_o \frac{\left(\frac{s}{\omega_z} + 1 \right)}{\left(\frac{s}{\omega_p} + 1 \right)} \begin{cases} \text{zero} = -\omega_z \\ \text{pole} = -\omega_p \end{cases} \quad (47)$$

Frequency response:

$$H(j\omega) = K_o \frac{\left(\frac{j\omega}{\omega_z} + 1 \right)}{\left(\frac{j\omega}{\omega_p} + 1 \right)} \quad (49)$$

Magnitude response :

$$|H(j\omega)| = |K_o| \frac{\sqrt{1 + \left(\frac{\omega}{\omega_z} \right)^2}}{\sqrt{1 + \left(\frac{\omega}{\omega_p} \right)^2}} \quad (50)$$

Magnitude plot: Magnitude response in dB:

$$|H(j\omega)|_{\text{dB}} = 20 \log|K_o| + 20 \log \sqrt{1 + \left(\frac{\omega}{\omega_z} \right)^2} - 20 \log|K_o| \sqrt{1 + \left(\frac{\omega}{\omega_p} \right)^2} \quad (51)$$

Let (\pm) sign refers to zero/pole terms. Straight line approximation is given by:


$$20 \log|K_o| \begin{cases} < 0 & |K_o| < 1 \\ = 0 & |K_o| = 1 \\ > 0 & |K_o| > 1 \end{cases} \quad (52)$$

$$\pm 20 \log \sqrt{1 + \left(\frac{\omega}{\omega_c} \right)^2} = \begin{cases} 0 & \omega \ll \omega_c \\ \pm 3 \text{ dB} & \omega = \omega_c \\ \pm 20 \log \left(\frac{\omega}{\omega_c} \right) & \omega \gg \omega_c \end{cases} \quad (53)$$

Phase plot: Phase response:

$$\phi(j\omega) = \tan^{-1} \left(\frac{\omega}{\omega_z} \right) - \tan^{-1} \left(\frac{\omega}{\omega_p} \right) \quad (54)$$
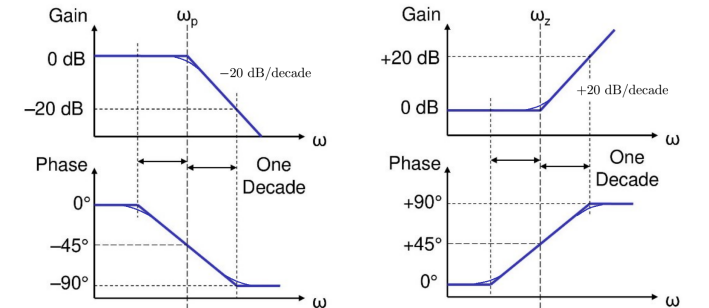
$$\phi(j\omega) \begin{cases} = 0^\circ & \omega < 0.1 \omega_c \\ = \pm 5.7^\circ & \omega = 0.1 \omega_c \\ = \pm 45^\circ & \omega = \omega_c \\ = \pm (90^\circ - 5.7^\circ) & \omega = 10 \omega_c \\ = \pm 90^\circ & \omega > 10 \omega_c \end{cases} \quad (55)$$



(48) Figure 19: Magnitude plot and phase plot (assume $|K_o| = 1$)

13 Common Source (CS) Amplifier

13.1 DC Biasing

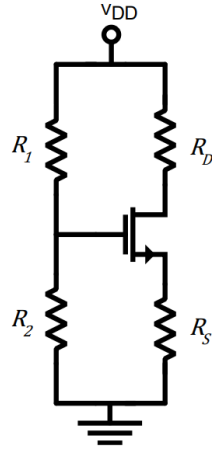


Figure 20

From circuit analysis :

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{DD} - I_D R_S \quad (56)$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S) \quad (57)$$

From the MOSFET characteristics curves :

$$I_D = k(V_{GS} - V_T)^2 \quad (58)$$

By solving, we get the DC biasing Q-point :

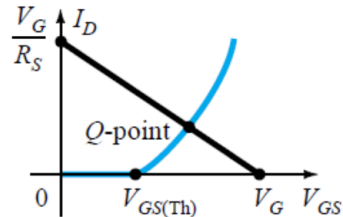


Figure 21

13.2 AC Amplifier Capacitance

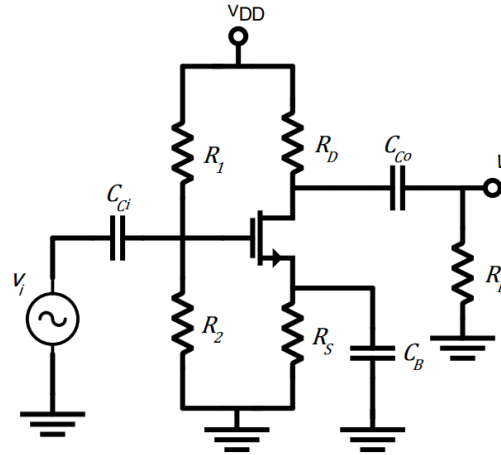


Figure 22

13.2.1 Capacitance Types

Coupling capacitors:

Block the DC, pass the AC

Bypass capacitors:

bypass the AC to the ground.

Internal capacitance:

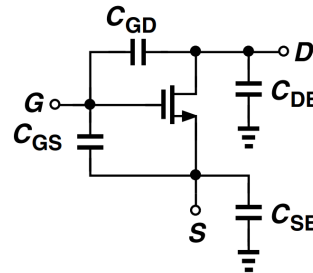


Figure 23: MOSFET internal capacitors

13.2.2 Capacitance Effect

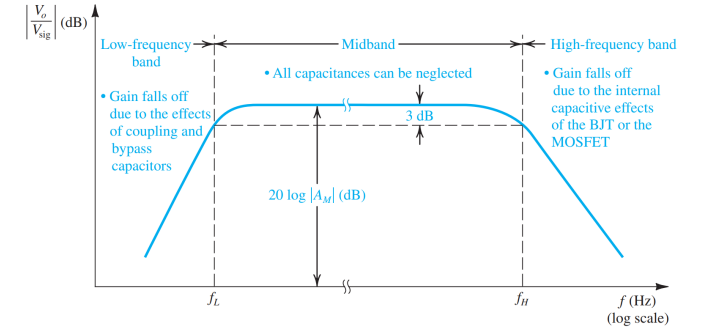


Figure 24

14 Frequency Response of a CS Amplifier

14.1 Low Frequency Response

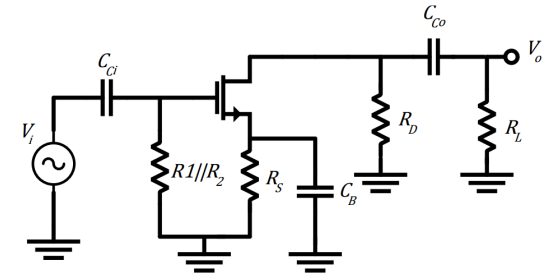


Figure 25

Transfer function :

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{V_o(s)}{I_d(s)} \times \frac{I_d(s)}{V_g(s)} \times \frac{V_g(s)}{V_i(s)}$$

The output circuit:

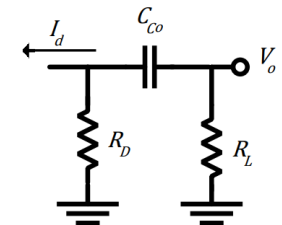


Figure 26

From current divider:

$$\frac{V_o(s)}{R_L} = -\frac{R_D}{R_D + \left(R_L + \frac{1}{sC_{co}}\right)} I_d(s)$$

$$\frac{V_o(s)}{I_d(s)} = \frac{-R_d || R_L}{1 + \frac{\omega_{p1}}{s}}$$

$$\omega_{p1} = \frac{1}{(R_D + R_L)C_{co}}$$

Pole $s_p = -\omega_{p1}$ and zero $s_z = 0$

The bypass circuit:

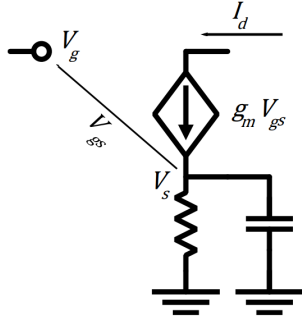


Figure 27

$$I_d(s) = g_m V_{gs}(s) = g_m V_g(s) - g_m I_d(s) \left(R_s || \frac{1}{sC_b}\right)$$

$$\frac{I_d(s)}{V_g(s)} = g_m \frac{1 + \frac{\omega_{z2}}{s}}{1 + \frac{\omega_{p2}}{s}}$$

$$\omega_{z2} = \frac{1}{R_s C_b} \quad \omega_{p2} = \frac{1 + g_m R_s}{R_s C_b}$$

Pole $s_p = -\omega_{p2}$ and zero $s_z = -\omega_{z2}$

The input circuit:

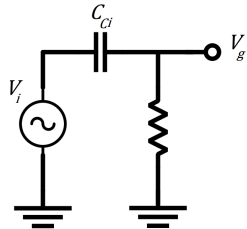


Figure 28

From voltage divider:

$$\frac{V_g(s)}{V_i(s)} = \frac{R_1 || R_2}{R_1 || R_2 + \frac{1}{sC_{ci}}} = \frac{1}{1 + \frac{\omega_{p3}}{s}} \quad (59)$$

$$\omega_{p3} = \frac{1}{(R_1 || R_2)C_{ci}}$$

Pole $s_p = -\omega_{p3}$ and zero $s_z = 0$

The overall transfer function:

$$H(s) = \frac{-R_D || R_L}{1 + \frac{\omega_{p1}}{s}} \times g_m \frac{1 + \frac{\omega_{z2}}{s}}{1 + \frac{\omega_{p2}}{s}} \times \frac{1}{1 + \frac{\omega_{p3}}{s}} \quad (62)$$

Frequency response:

$$H(j\omega) = H(s)|_{s=j\omega}$$

Bode plot:

Assume $\omega_{z2} < \omega_{p1} < \omega_{p2} < \omega_{p3}$

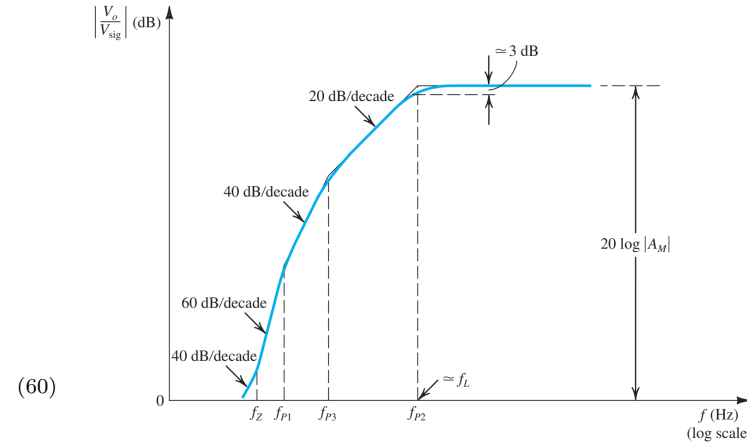


Figure 29

14.2 Mid Band Gain:

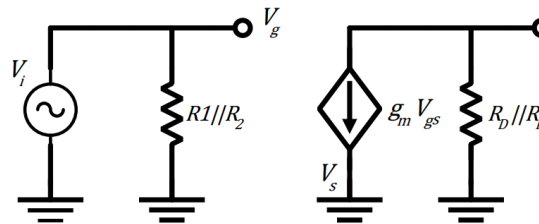


Figure 30

Resolve the circuit or substitute in Equation ?? with $s = \infty$

$$A_M = \frac{v_d}{v_g} = -g_m R_D || R_L \quad (63)$$

14.3 High Frequency Response

We consider the effect of internal transistor capacitance

14.3.1 Miller's Theorem

A method that transforms a floating impedance (Z_f) to two grounded impedances.

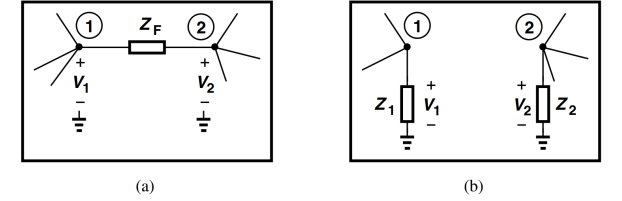


Figure 31: (a) General circuit including a floating impedance, (b) equivalent of (a) as obtained from Miller's theorem.

$$Z_1 = \frac{Z_f}{1 - A_v} \quad Z_2 = \frac{Z_f}{1 - \frac{1}{A_v}} \quad (64)$$

$$A_v = \frac{V_2}{V_1}$$

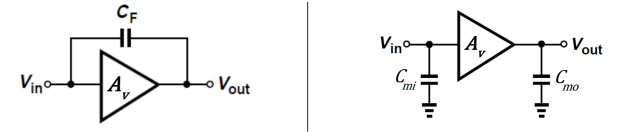


Figure 32

$$C_{mi} = C_F(1 - A_M) \quad C_{mo} = C_F \left(1 - \frac{1}{A_M}\right) \quad (65)$$

A_M : Mid band gain.

Miller approximation :

$$A_v(s) \approx A_M \quad (66)$$

Circuit analysis:

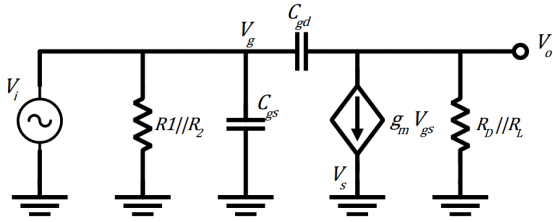


Figure 33

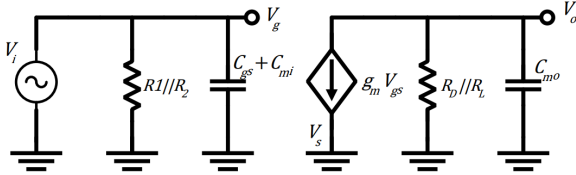


Figure 34

Transfer function:

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{V_o(s)}{V_{gs}(s)} \times \frac{V_{gs}(s)}{V_i(s)}$$

Input circuit:

$$\frac{V_{gs}}{V_i} = 1$$

Output circuit:

$$V_o(s) = -g_m V_{gs} \left(R_D || R_L || \frac{1}{sC_{mo}} \right)$$

$$\frac{V_o(s)}{V_i(s)} = - \frac{g_m (R_D || R_L)}{1 + \frac{s}{\omega_H}}$$

$$\omega_H = \frac{1}{(R_D || R_L) C_{om}}$$

Frequency response:

$$H(j\omega) = H(s)|_{s=j\omega}$$

Transfer function:

$$H(s) = - \frac{g_m (R_D || R_L)}{1 + \frac{s}{\omega_H}}$$

Pole $s_{pH} = -\omega_H$

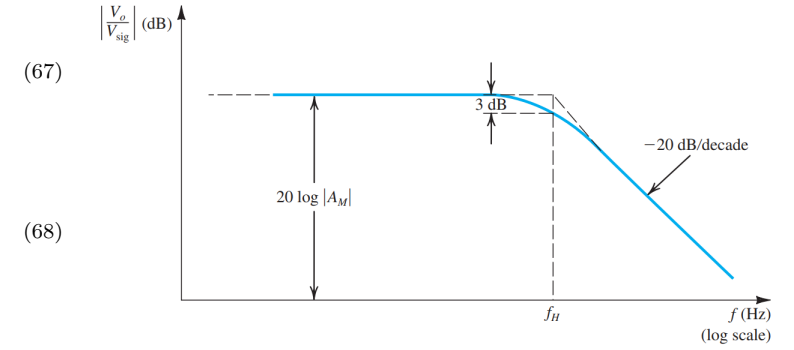


Figure 35: High frequency response

(67)

(68)

(69)