

EEC 233 : Electronics II ¹

Part 1

1 Bipolar Junction Transistor (BJT)

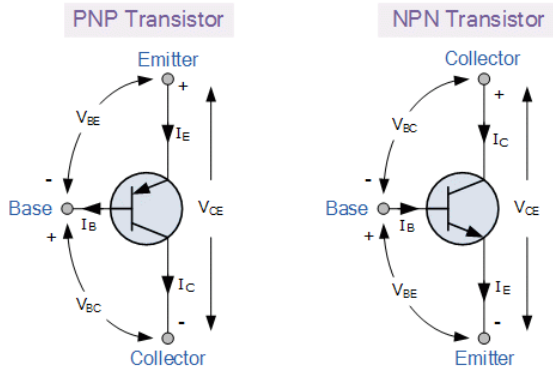


Figure 1

$$I_E = I_B + I_C \quad (1)$$

For active mode:

$$I_C = \beta I_B \quad (2)$$

$$I_C = \alpha I_E \approx I_E \quad (3)$$

$$I_B = \frac{I_E}{\beta + 1} \quad (4)$$

$$\beta = \frac{\alpha}{1 - \alpha} \quad (5)$$

$$\alpha = \frac{\beta}{\beta + 1} \quad (6)$$

$$r_o = \frac{V_A}{I_C} \quad (7)$$

r_o : Output resistance.

V_A : Early voltage.

¹Taha Ahmed

2 Current Mirror

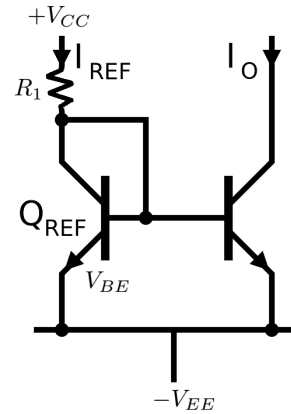


Figure 2

$$\frac{I_{ref}}{I_o} = \frac{1}{1 + \frac{2}{\beta}} \approx 1 \quad (8)$$

$$I_o = \frac{V_{EE} + V_{CC} - V_{BE}}{R_1}$$

3 Multiple Current Mirror

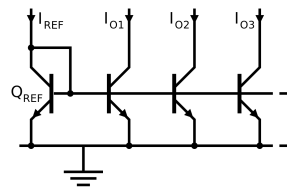


Figure 3

$$\frac{I_o}{I_{ref}} = \frac{1}{1 + \frac{(N+1)}{\beta}} \quad (10)$$

4 Modified Multiple Current Mirror

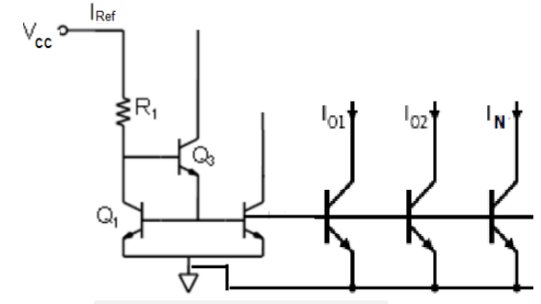


Figure 4

$$\frac{I_o}{I_{ref}} = \frac{1}{1 + \frac{(N+1)}{\beta^2}} \quad (11)$$

$$I_o = \frac{V_{EE} + V_{CC} - 2V_{BE}}{R_1} \quad (12)$$

5 Differential Amplifiers

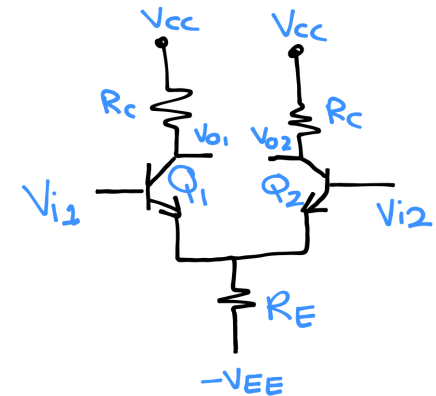


Figure 5

5.1 DC Analysis

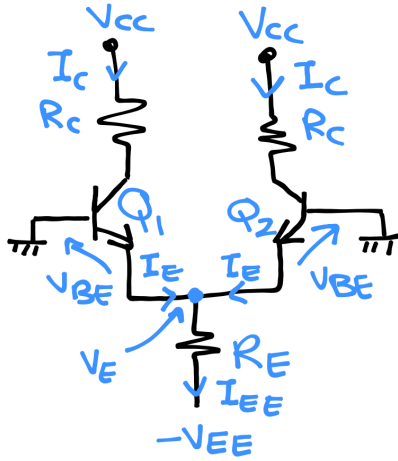


Figure 6

$$V_E = -V_{BE} \quad (13)$$

$$I_{EE} = \frac{V_{EE} - V_{BE}}{R_E} \quad (14)$$

$$I_E = \frac{1}{2} I_{EE} = \frac{V_{EE} - V_{BE}}{2R_E} \quad (15)$$

$$I_C = \alpha I_E \approx I_E \quad (16)$$

$$V_C = V_{CC} - I_C R_C \quad (17)$$

5.2 AC Analysis : Common mode

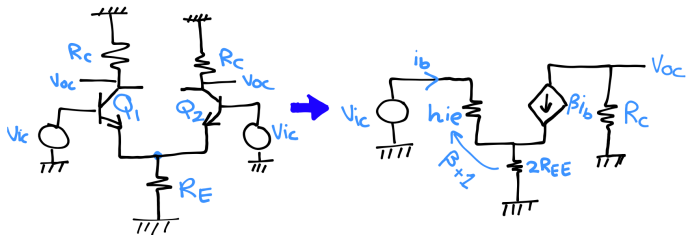


Figure 7

5.3 AC Analysis : Difference Mode

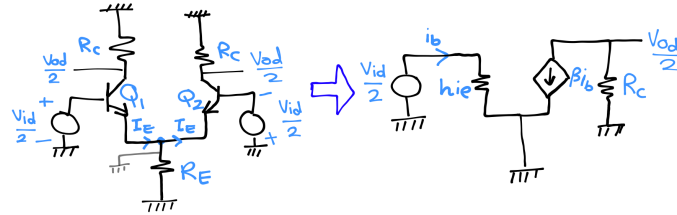


Figure 8

$$A_d = \frac{V_{od}}{V_{id}} = \frac{-\beta R_C}{h_{ie}} \quad (21)$$

$$R_{in} = h_{ie} \quad (22)$$

$$R_{id} = 2R_{in} = 2h_{ie} \quad (23)$$

Common mode rejection ratio:

$$\text{CMRR} = 20 \log_{10} \left| \frac{A_d/2}{A_c} \right| \text{ dB} \quad (24)$$

6 Multistage Differential Amplifier

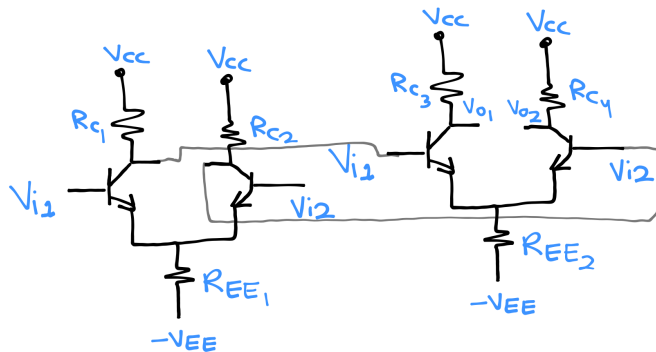


Figure 9

6.1 DC Analysis

$$I_{EE1} = \frac{V_{EE} - V_{BE}}{R_{EE1}} \quad (25)$$

$$I_{EE2} = \frac{V_{EE} + V_{CC} - I_{C1} R_{C1} - V_{BE}}{R_{EE1}} \quad (26)$$

6.2 AC Analysis : Common Mode

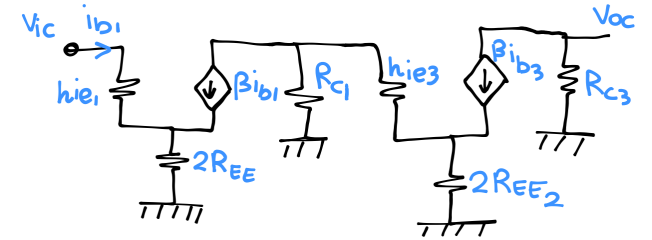


Figure 10

$$A_C = \frac{V_{oc}}{V_{ic}} = \frac{\beta^2 R_{C1} R_{C3}}{(h_{ie1} + \beta \times 2R_{EE}) \times (R_{C1} + h_{ie3} + \beta \times 2R_{EE})} \quad (27)$$

6.3 AC Analysis : Difference Mode

Substitute with $R_{EE1} = 0$ and $R_{EE2} = 0$

$$A_C = \frac{V_{od}}{V_{id}} = \frac{\beta^2 R_{C1} R_{C3}}{h_{ie1} \times (R_{C1} + h_{ie3})} \quad (28)$$

Common mode rejection ratio:

$$\text{CMRR} = 20 \log_{10} \left| \frac{A_d/2}{A_c} \right| \text{ dB}$$

7 MOSFET

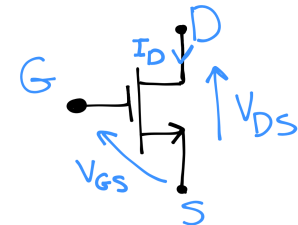


Figure 11: N-channel E-MOSFET

$$I_G = 0 \quad (29)$$

$$I_D = \frac{1}{2} K'_n \times \frac{W}{L} \times (V_{GS} - V_T)^2 \quad (30)$$

$$g_m = \frac{\partial I_d}{\partial V_{GS}} = K'_n \times \frac{W}{L} \times (V_{GS} - V_T) \quad (31)$$

Solving the quadratic equation, consider the solution such that $V_{GS} > V_T$

8 Current Mirror Using MOSFET

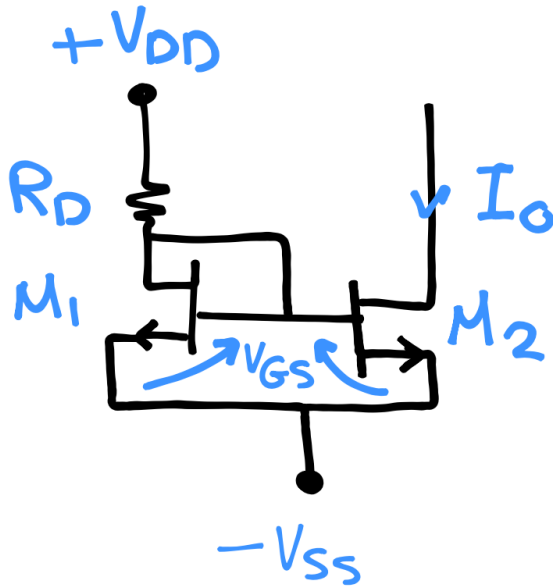


Figure 12

$$\frac{I_{ref}}{I_o} = \frac{(W/L)_1}{(W/L)_2}$$

Design equation:

$$I_{ref} = \frac{V_{SS} + V_{DD} - V_{GS}}{R_D} \quad (33)$$

9 Differential Amplifier Using MOSFET

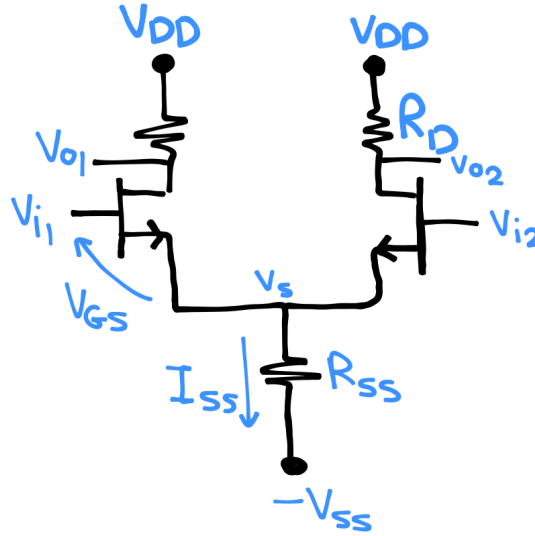


Figure 13

9.1 DC Analysis

$$I_{SS} = \frac{V_{SS} - V_{GS}}{R_{SS}} \quad (34)$$

$$I_D = \frac{I_{SS}}{2} = \frac{V_{SS} - V_{GS}}{2R_{SS}} \quad (35)$$

$$I_D = K_n (V_{GS} - V_T)^2 \quad (36)$$

Such that $K_n = \frac{1}{2} K'_n \times \frac{W}{L}$.
Solve 35 with 36 to get V_{GS}

$$g_m = K'_n \times \frac{W}{L} \times (V_{GS} - V_T)$$

9.2 AC Analysis : Common mode

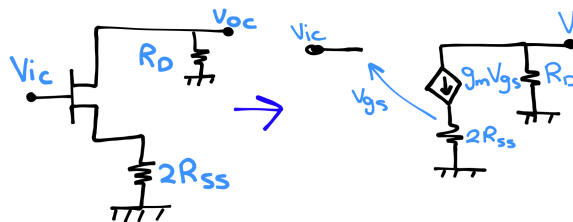


Figure 14

$$A_C = \frac{V_{OC}}{V_{IC}} = \frac{-g_m R_d}{1 + 2g_m R_{SS}} \quad (37)$$

9.3 AC Analysis : Difference Mode

Substitute with $R_{SS} = 0$

$$A_d = -g_m R_D \quad (38)$$

Common mode rejection ratio:

$$\text{CMRR} = 20 \log_{10} \left| \frac{A_d/2}{A_c} \right| \text{ dB}$$

10 DC Level Shifting

When $v_i = 0$, v_o must be zero.
If $v_o \neq 0$, it is called DC offset.

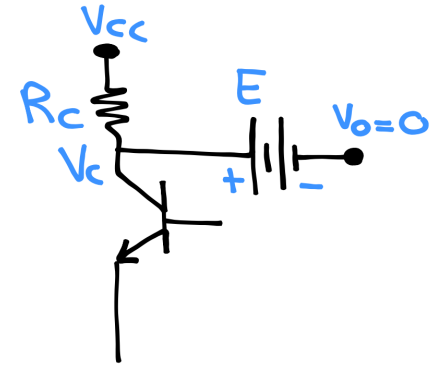


Figure 15: Put a DC source, $|v_c| = |E|$ in opposite directions

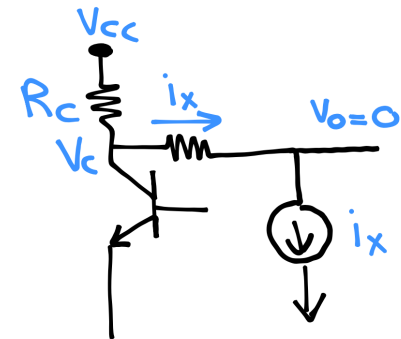


Figure 16: $v_o = v_c - i_x R_x$

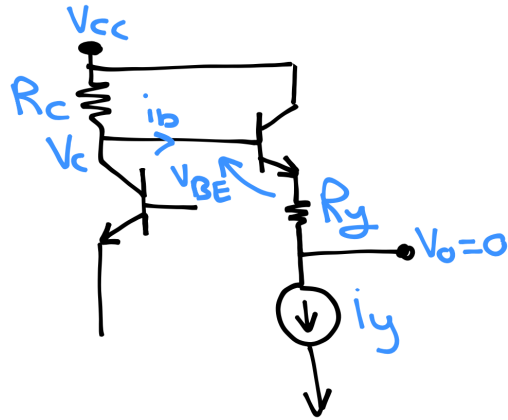


Figure 17: $v_o = v_c - V_{BE} - i_y R_y$

11.1 Non Inverting Amplifier

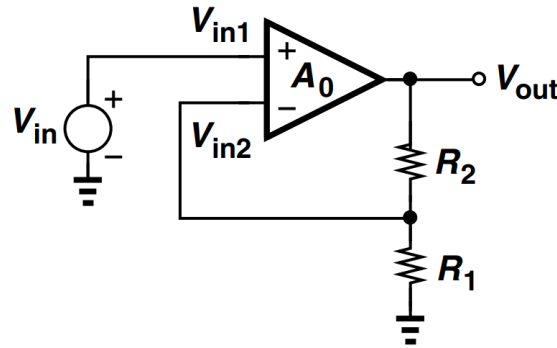


Figure 19

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1} \quad (39)$$

11.2 Inverting Amplifier

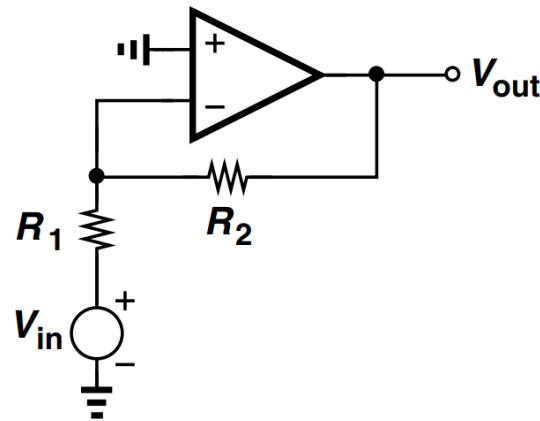


Figure 20

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \quad (40)$$

11.3 Summing Amplifier

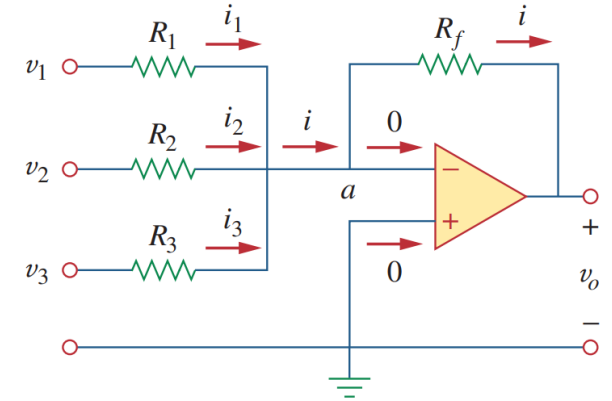


Figure 21

$$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right) \quad (41)$$

11.4 Summing Non Inverting Amplifier

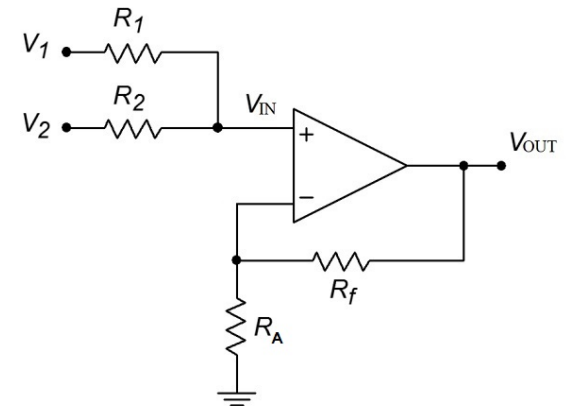


Figure 22

$$V_{out} = V_1 \frac{R_2}{R_1 + R_2} \left(1 + \frac{R_f}{R_a}\right) + V_2 \frac{R_1}{R_1 + R_2} \left(1 + \frac{R_f}{R_a}\right) \quad (42)$$

11 Operational Amplifiers

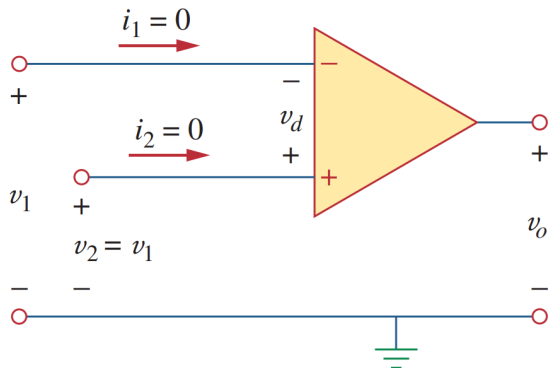


Figure 18: Ideal op amp model.

11.5 Difference Amplifier

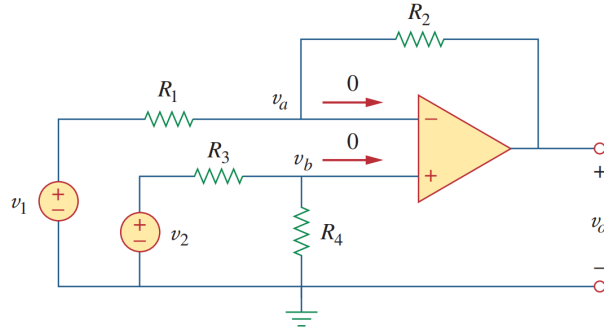


Figure 23

$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)}v_2 - \frac{R_2}{R_1}v_1 \quad (43)$$

if $\frac{R_1}{R_2} = \frac{R_3}{R_4}$ op amp circuit is a difference amplifier, Equation 43 becomes

$$v_o = \frac{R_2}{R_1}(v_2 - v_1) \quad (44)$$

11.6 Instrumentation Amplifier

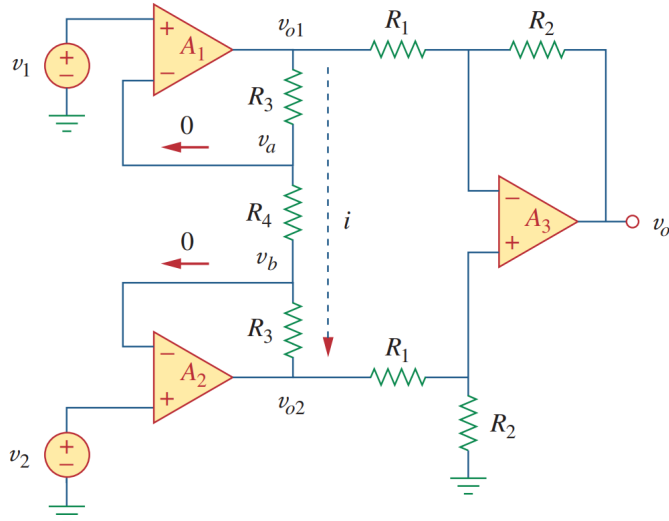


Figure 24

11.7 Integrator

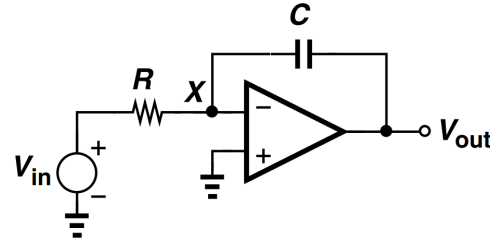


Figure 25

$$V_{out} = -\frac{1}{RC} \int V_{in} dt \quad (46)$$

$$\therefore \frac{\Delta V_o}{\Delta t} = -\frac{E}{RC} \quad (47)$$

11.7.1 Triangular Wave generator

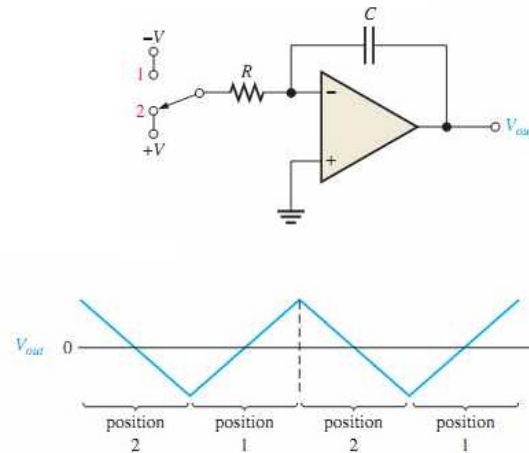


Figure 26: Triangular wave oscillator - Output voltage as the switch is thrown back and forth at regular intervals

Another way to generate triangular wave is discussed in Subsection 13.4.

11.7.2 Sawtooth Wave generator

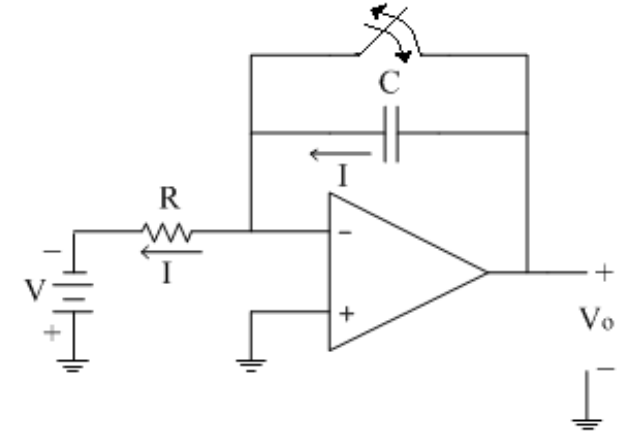


Figure 27: Sawtooth wave generator

11.8 Differentiator

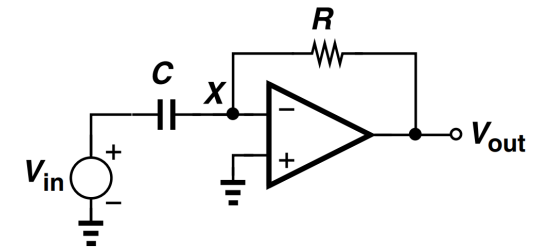


Figure 28

$$V_{out} = -RC \frac{dV_{in}}{dt} \quad (48)$$

12 Converters

12.1 Voltage to Current Converters

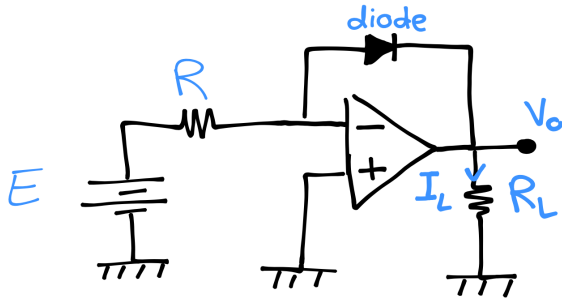


Figure 29

$$I_D = \frac{E}{R} \quad (49)$$

$$V_o = -0.7 \text{ Volt} \quad (50)$$

$$I_L = \frac{V_o}{R_L} \quad (51)$$

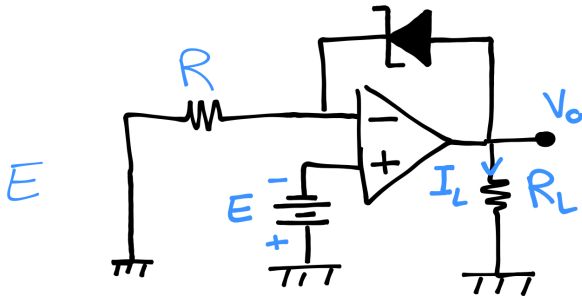


Figure 30

$$V_o = -E - V_z \quad (52)$$

$$I_L = \frac{V_o}{R_L} \quad (53)$$

V_z : Zener voltage.

We don't want I_L to be dependent of the load R_L

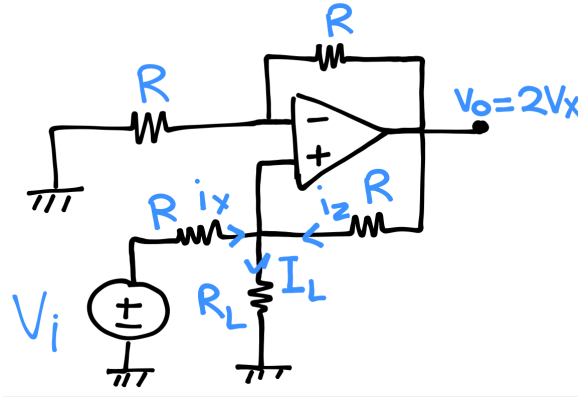


Figure 31: Constant current source

$$I_L = \frac{V_i}{R} \quad (54)$$

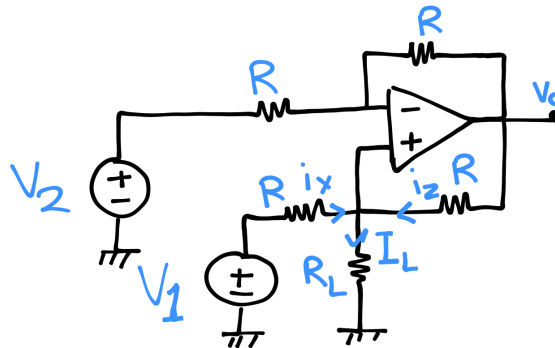


Figure 32: Constant current source - Voltage to current converter

$$I_L = \frac{V_1 - V_2}{R} \quad (55)$$

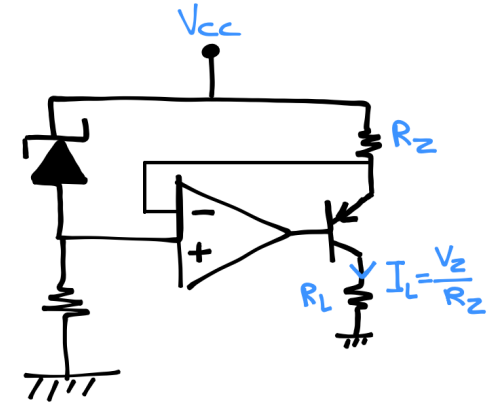


Figure 33: Constant high current source with grounded load

12.2 Current to Voltage Converters

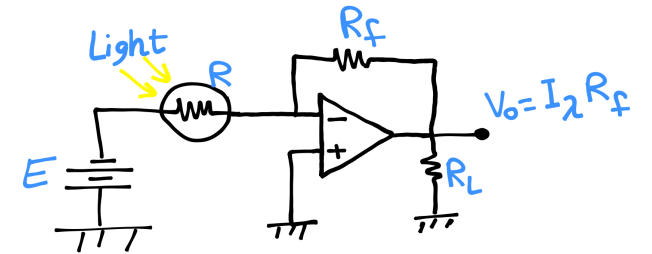


Figure 34

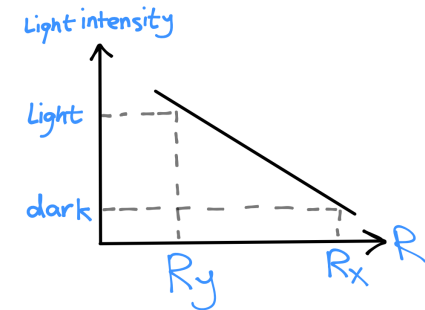


Figure 35

$$V_o = I_L R_f \quad (56)$$

12.4 Phase Shifter Circuit

$$I_\lambda = \frac{E}{\text{photo resistance}} \quad (57)$$

12.3 Basic Bridge Circuit

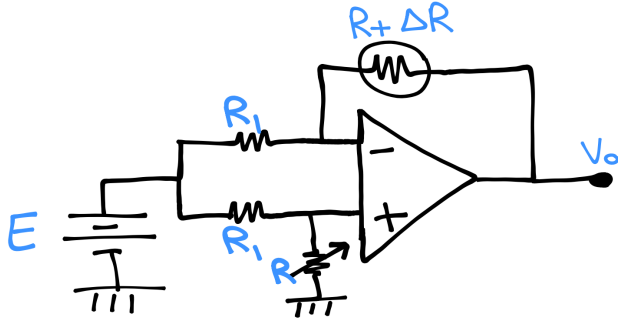


Figure 36

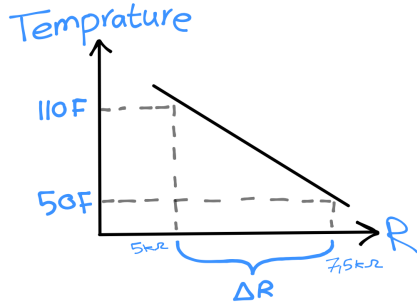


Figure 37

$$V_o = \frac{-\Delta R}{R_1 + R} E \quad (58)$$

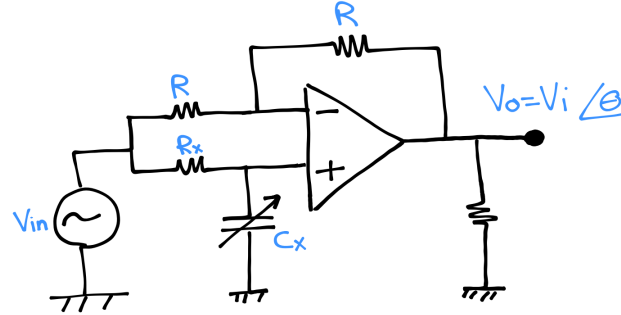


Figure 38

From superposition:

$$V_o = V_{o1} + V_{o2}$$

$$V_{o1} = -V_i$$

$$V_{o2} = 2V_x = 2V_i \frac{\frac{1}{j\omega C_x}}{R_x + \frac{1}{j\omega C_x}} = 2V_i \frac{1}{1 + j\omega C_x R_x}$$

$$\therefore V_o = \frac{2V_i}{1 + j\omega C_x R_x} - V_i = V_i \times \frac{2 - (1 + j\omega C_x R_x)}{1 + j\omega C_x R_x}$$

$$\therefore \frac{V_o}{V_i} = \frac{1 - j\omega C_x R_x}{1 + j\omega C_x R_x}$$

$$\left| \frac{V_o}{V_i} \right| = 1 \quad (\text{unity gain}) \quad (59)$$

$$\theta = \frac{-\tan^{-1}(\omega C_x R_x)}{+\tan^{-1}(\omega C_x R_x)} = -2 \tan^{-1}(\omega C_x R_x) \quad (60)$$

$$\therefore -\frac{\theta}{2} = \tan^{-1}(\omega C_x R_x)$$

$$\therefore \omega C_x R_x = -\tan\left(\frac{\theta}{2}\right) \quad (61)$$

13 Operational Amplifier Applications

13.1 Negative Impedance Circuit

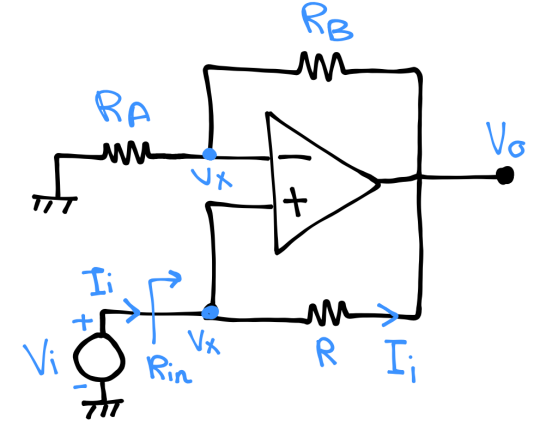


Figure 39

$$R_{in} = \frac{V_i}{I_i} = -\frac{R_A R}{R_B} \quad (62)$$

If R is replaced by Z , the circuit develops negative impedance.

(e.g. if replaced by a capacitor, it develops $-ve \times -ve =$ positive impedance)

13.2 Dependent Current Generator

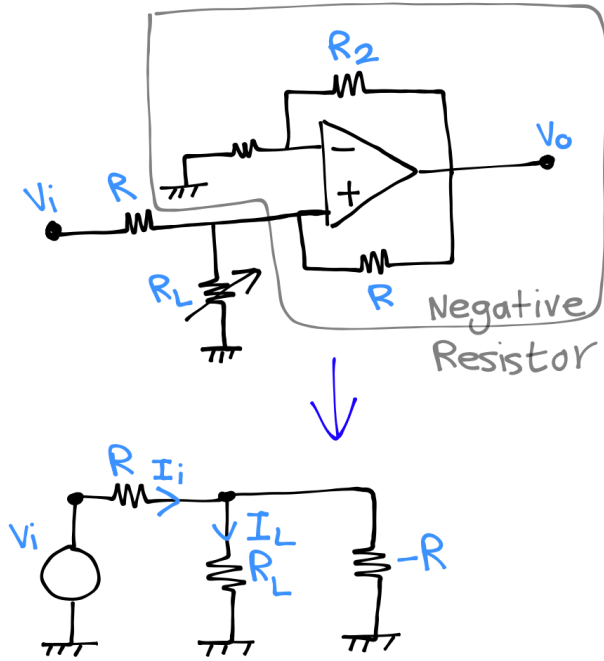


Figure 40

$$I_L = \frac{V_i}{R + R_L || -R} = \frac{V_i}{R + \frac{-R_L R}{R_L - R}} = \frac{V_i(R_L - R)}{-R^2}$$

From current divider :

$$I_L = I_i \frac{-R}{R_L - R} = \frac{V_i(R_L - R)}{-R^2} \times \frac{-R}{R_L - R}$$

$$\therefore I_L = \frac{V_i}{R} \quad (63)$$

Doesn't depend on the load, it is considered as voltage to current converter.

13.3 Non Inverting Miller Integrator

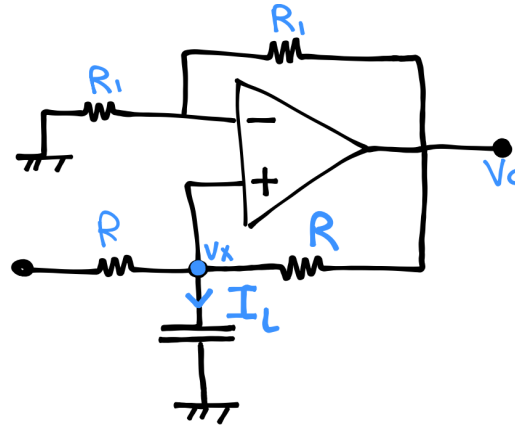


Figure 41

From Equation 63 :

$$I_L = \frac{V_i}{R}$$

$$V_o = V_x \left(1 + \frac{R}{R} \right) = 2V_x$$

$$V_x = V_c = \frac{1}{C} \int I_L dt = \frac{1}{C} \int \frac{V_i}{R} dt$$

$$\therefore V_o(t) = \frac{2}{RC} \int V_i dt \quad (64)$$

Notice that there are no negative sign, unlike the integrator discussed in Subsection 11.7.

13.4 Triangular Wave Oscillator

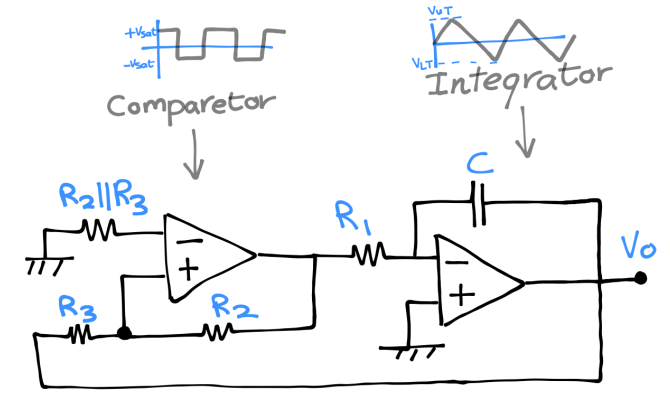


Figure 42

$$V_{\text{upper limit}} = +V_{\text{saturation}} \times \frac{R_3}{R_2} \quad (65)$$

$$V_{\text{lower limit}} = -V_{\text{saturation}} \times \frac{R_3}{R_2} \quad (66)$$

$$f = \frac{1}{4R_1 C} \times \frac{R_2}{R_3} \quad (67)$$

f : frequency of oscillations.

Another way to generate triangular wave is discussed in Subsubsection 11.7.1.

13.5 Square Wave Oscillator

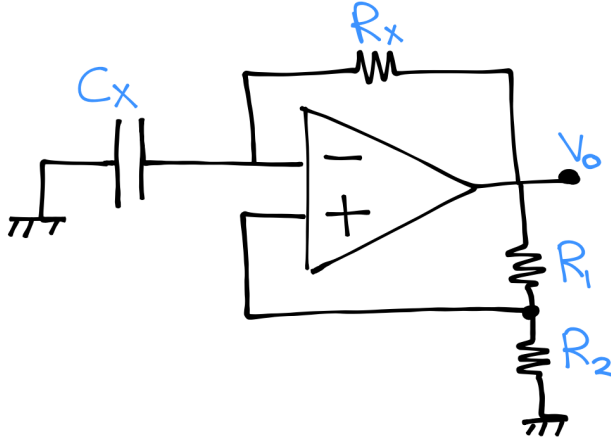


Figure 43

$$V_{\text{upper limit}} = +V_{\text{saturation}} \times \frac{R_2}{R_1 + R_2} \quad (68)$$

$$V_{\text{lower limit}} = -V_{\text{saturation}} \times \frac{R_2}{R_1 + R_2} \quad (69)$$

$$T = 2\tau \ln \left(\frac{1 + \beta}{1 - \beta} \right) \quad (70)$$

$$f = \frac{1}{T} \quad (71)$$

$$\tau = R_x C_x \quad (72)$$

$$\beta = \frac{R_2}{R_1 + R_2} \quad (73)$$

13.6 Voltage Comparator (Saturation Comparator)

We operate the op-amp in the open loop mode depending on the high open loop gain $A \approx \infty$ to drive the op-amp into saturation.

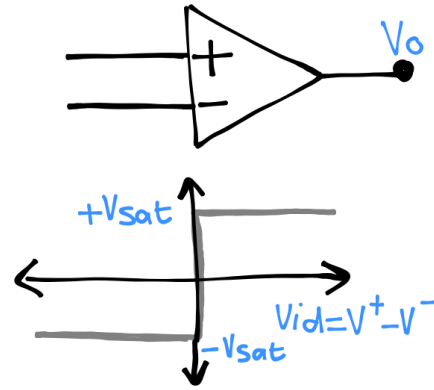


Figure 44

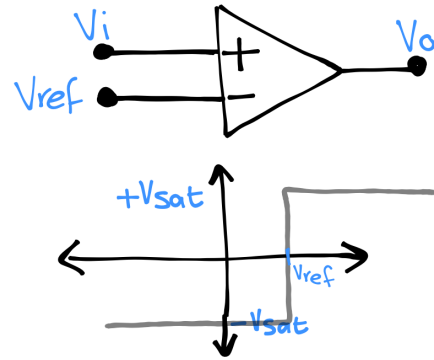


Figure 45

$$V_o = \begin{cases} +V_{\text{sat}} & V_i > V_{\text{ref}} \\ 0 & V_i = V_{\text{ref}} \\ -V_{\text{sat}} & V_i < V_{\text{ref}} \end{cases} \quad (74)$$

13.7 Zero Voltage Comparator

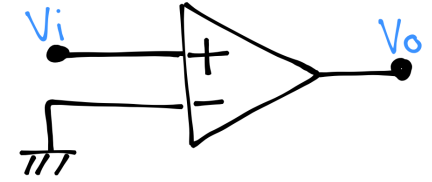


Figure 46

$$V_{\text{ref}} = 0$$

$$V_o = \begin{cases} +V_{\text{sat}} & V_i > 0 \\ 0 & V_i = 0 \\ -V_{\text{sat}} & V_i < 0 \end{cases} \quad (75)$$

The output toggles when the input crosses zero

13.8 Voltage (Saturation) Comparator With Inverting Op-Amp

Connect V_i to the inverting terminal to invert the functionality of the comparator

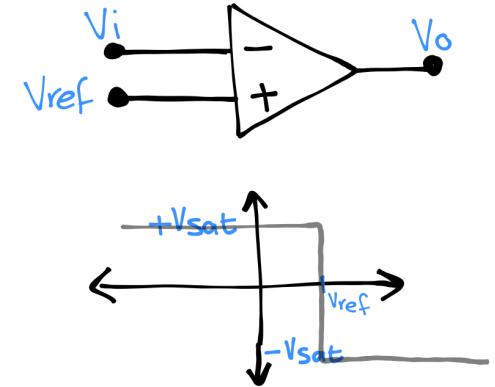


Figure 47

$$V_o = \begin{cases} -V_{\text{sat}} & V_i > V_{\text{ref}} \\ 0 & V_i = V_{\text{ref}} \\ +V_{\text{sat}} & V_i < V_{\text{ref}} \end{cases} \quad (76)$$

13.8.1 Control Street Light

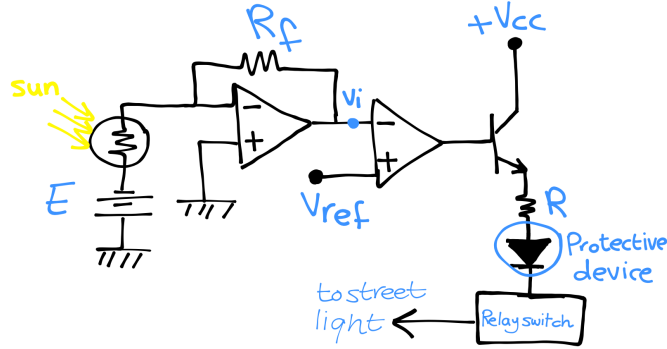


Figure 48

13.9 Comparator With Bounded Output

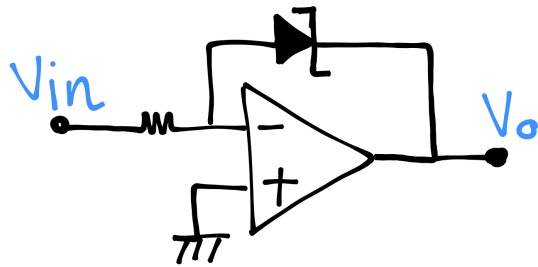


Figure 49

The operation is as follows, since the anode of the zener is connected to the inverting (−) input, it is a virtual ground (= 0 V). Therefore, when the output voltage reaches a positive value equals to the zener voltage, it limits at that value. When the output switches negative, the zener acts as regular diode and becomes forward biased at 0.7 V, limiting the negative output to that value. Turning the zener around limits the output voltages in the opposite direction

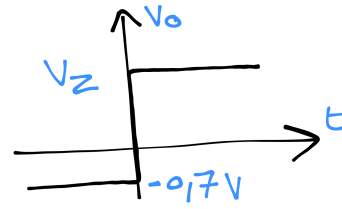


Figure 50

Two Zener diodes arranged as shown in Figure 51 limit the output voltage to the zener voltage plus the forward voltage drop (0.7 V) of the forward biased zener both positively and negatively

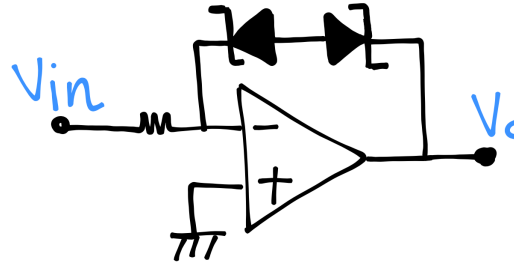


Figure 51

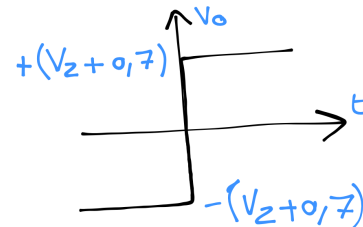


Figure 52

13.10 Schmitt Trigger

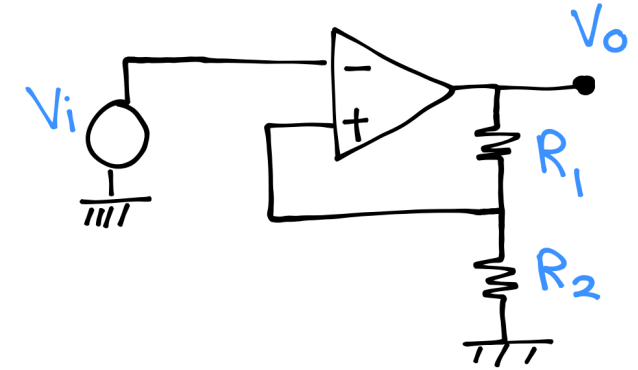


Figure 53

Made with positive feedback to eliminate the effect of noise.

Upper threshold voltage is the input voltage V_i when the output voltage V_o equals $V_{\text{saturation}}$.

Similarly, lower threshold voltage is the input voltage V_i when the output voltage V_o equals $-V_{\text{saturation}}$.

$$V_{\text{upper threshold}} = +V_{\text{sat}} \frac{R_2}{R_1 + R_2} \quad (77)$$

$$V_{\text{lower threshold}} = -V_{\text{sat}} \frac{R_2}{R_1 + R_2} \quad (78)$$

$$V_o = \begin{cases} -V_{\text{sat}} & V_i > V_{\text{upper threshold}} \\ \text{No change} & V_{\text{lower threshold}} < V_i < V_{\text{upper threshold}} \\ +V_{\text{sat}} & V_i < V_{\text{lower threshold}} \end{cases} \quad (79)$$

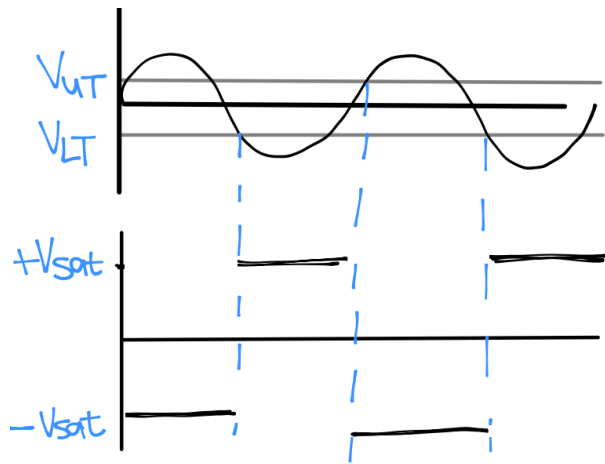


Figure 54

Another design of the schmitt trigger:

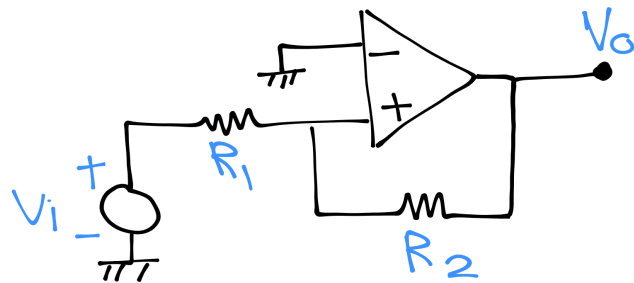


Figure 55

Note that :

$$R_2 > R_1$$

$$V_o = \begin{cases} +V_{sat} & V_i > \frac{R_1}{R_2} V_{sat} \\ \text{No change} & -\frac{R_1}{R_2} V_{sat} < V_i < \frac{R_1}{R_2} V_{sat} \\ -V_{sat} & V_i < -\frac{R_1}{R_2} V_{sat} \end{cases} \quad (80)$$

13.10.1 Schmitt Trigger With Reference

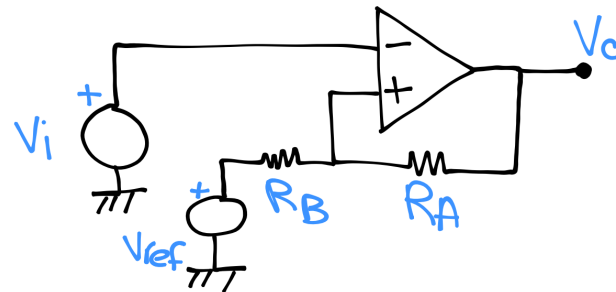


Figure 56

$$V_{UT} = V_{ref} + \frac{+V_{sat} - V_{ref}}{R_A + R_B} R_B \quad (81)$$

$$V_{LT} = V_{ref} + \frac{-V_{sat} - V_{ref}}{R_A + R_B} R_B \quad (82)$$

$$V_o = \begin{cases} -V_{sat} & V_i > V_{UT} \\ \text{No change} & V_{LT} < V_i < V_{UT} \\ +V_{sat} & V_i < V_{LT} \end{cases} \quad (83)$$

13.11 Window Comparetor

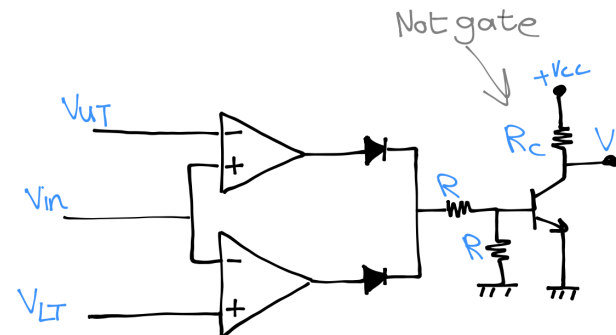


Figure 57

$$V_o \text{ (on) when } V_{LT} < V_i < V_{UT} \quad (84)$$

13.12 Logarithmic Amplifier

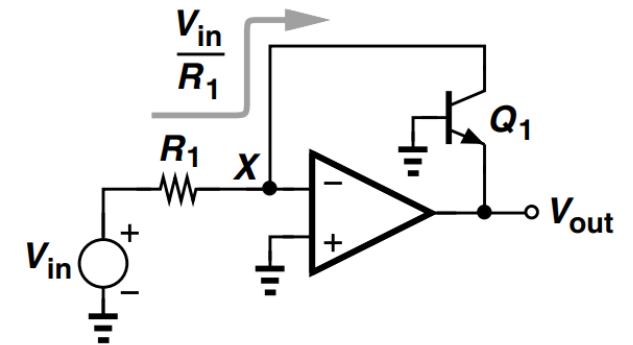


Figure 58

$$V_{out} = -V_{BE}$$

$$V_{out} = -V_T \ln \left(\frac{V_{in}}{R_1 I_S} \right) = -K \ln(V_{in}) \quad (85)$$

I_S : Saturation current.

K : constant.

The output is therefore proportional to the natural logarithm of V_{in}

Contents		12 Converters	6
1 Bipolar Junction Transistor (BJT)	1	12.1 Voltage to Current Converters	6
2 Current Mirror	1	12.2 Current to Voltage Converters	6
3 Multiple Current Mirror	1	12.3 Basic Bridge Circuit	7
4 Modified Multiple Current Mirror	1	12.4 Phase Shifter Circuit	7
5 Differential Amplifiers	1	13 Operational Amplifier Applications	7
5.1 DC Analysis	2	13.1 Negative Impedance Circuit	7
5.2 AC Analysis : Common mode	2	13.2 Dependent Current Generator	8
5.3 AC Analysis : Difference Mode	2	13.3 Non Inverting Miller Integrator	8
6 Multistage Differential Amplifier	2	13.4 Triangular Wave Oscillator	8
6.1 DC Analysis	2	13.5 Square Wave Oscillator	9
6.2 AC Analysis : Common Mode	2	13.6 Voltage Comparator (Saturation Comparator)	9
6.3 AC Analysis : Difference Mode	2	13.7 Zero Voltage Comparator	9
7 MOSFET	2	13.8 Voltage (Saturation) Comparator With In-	9
8 Current Mirror Using MOSFET	3	verting Op-Amp	9
9 Differential Amplifier Using MOSFET	3	13.8.1 Control Street Light	10
9.1 DC Analysis	3	13.9 Comparator With Bounded Output	10
9.2 AC Analysis : Common mode	3	13.10Schmitt Trigger	10
9.3 AC Analysis : Difference Mode	3	13.10.1 Schmitt Trigger With Reference	11
10 DC Level Shifting	3	13.11Window Comparator	11
11 Operational Amplifiers	4	13.12Logarithmic Amplifier	11
11.1 Non Inverting Amplifier	4		
11.2 Inverting Amplifier	4		
11.3 Summing Amplifier	4		
11.4 Summing Non Inverting Amplifier	4		
11.5 Difference Amplifier	5		
11.6 Instrumentation Amplifier	5		
11.7 Integrator	5		
11.7.1 Triangular Wave generator	5		
11.7.2 Sawtooth Wave generator	5		
11.8 Differentiator	5		