

EEC 242 - VHDL cheat sheet¹

1 Chapter 1

- VHDL \Rightarrow **V**ery **H**igh **S**peed **I**ntegrated **C**ircuits **H**ardware **D**escription **L**anguage
- VHDL is a concurrent language.
- VHDL is not case sensitive.
- Purpose:
 - Documentation
 - Simulation
- Documentation : write a comment
Characters "- -"

1.1 Entity

- Entity declaration defines the name of the entity and lists the input and output ports.

```
entity example1 is
    port(x1, x2, x3 :in std_logic;
          in1       :in integer;
          val1      :out std_logic;
          val2      :out std_logic_vector(3 downto 0))
end example1;
```

1.1.1 Signals Names

- Signal Name specifies external interface signals
- It can be any alphanumeric character
- Rules:
 - Must begin with a letter (Don't begin with number or _)
 - Don't end with underscore _
 - No two successive underscores __

1.1.2 Modes

- Indicate signal direction:
 - in : input
 - out : output(whose value can only be read by other entities)
 - buffer output(whose value can be read inside the entity's architecture)
 - inout : can be an input or an output.

1.1.3 Types

- A built in or user defined signal type:
 - bit : 0 or 1.
 - bit_vector : vector of bits.
 - std_logic : 0, 1, Z, -, L, H, U, X, W.
 - std_logic_vector : vector of std_logics.
 - boolean : TRUE or FALSE.
 - integer : 0 or 1.
 - real : 0 or 1.
 - character : character.
 - time : time.
- bit & bit_vector :

¹Taha Ahmed

- bit : 0 or 1.
- `port (C : in bit;
 BYTE : in bit));`
- bit_vector : multi-bit data
- Difference between to and downto


```
port (to_example : out bit_vector(1 to 8);
      downto_example : out bit_vector(7 downto 0));
```
- to_example <= "10011000" results in


```
to_example(1) = 1
to_example(2) = 0
to_example(3) = 0
to_example(4) = 1
to_example(5) = 1
to_example(6) = 0
to_example(7) = 0
to_example(8) = 0
```
- downto_example <= "10011000" results in


```
downto_example(7) = 1
downto_example(6) = 0
downto_example(5) = 0
downto_example(4) = 1
downto_example(3) = 1
downto_example(2) = 0
downto_example(1) = 0
downto_example(0) = 0
```

- std_logic & std_logic_vector.

- to use this type


```
Library IEEE;
Use IEEE.std_logic_1164.all;
```
- 1
0
Z: high impedance
-: don't care
U: uninitialized
X: unknown
W: weak unknown
L: weak high
H: weak low

- Integer:

- represents a binary number
- by default, it has 32 bits, range from $-(2^{31} - 1)$ to $2^{31} - 1$.
- you can declare integer with fewer bits by Range keyword :


```
Integer Range -127 to 127;
```

- Generic:

- `entity example1 is`

```
Generic (Delay : Time := 10ns);
port(x1, x2, x3 :in std_logic;
     in1 :in std_logic;
     in2 :in std_logic;
     output :out std_logic;
     val2 :out std_logic_vector(3 downto 0))
end example1;
Architecture Behavior of example1 is
begin
```

```

...
output <= in1 or in2 after Delay;
...
end Behavior;
entity CPU is
    Generic (BusWidth : Integer := 16);
    port(
        DataBus : inout std_logic_vector (BusWidth downto 0));
end Cpu;

```

1.2 Architecture

- specifies how the circuit operates and how it is implemented.
- Ways
 - Behavioral (Data flow / Sequential)
 - Structural
 - Combination of both

1.2.1 Operators

- From Highest Precedence to Lowest:

** : exponentiation

ABS

Not

*

/

MOD

REM

+

-

& : Concatenation

=

/= : Not equal

<

<=

>

>=

AND

OR

NAND

NOR

XOR

XNOR

NOT

```

entity example1 is
    port(x1, x2, x3 :in std_logic;
        output :out std_logic);
end example1;

```

```

Architecture Behavior of example1 is
begin

```

```

    output <= (x1 and x2) or ( not x2 and x3);

```

```

end Behavior;

```

1.2.2 Signals

- Represents logic signals or wires in a circuit.
- Signals assignment operator <=

- Signal signal_name : type;
- **entity example1 is**
 port(x1, x2, x3 :in std_logic;
 output :out std_logic);
end example1;

Architecture Behavior of example1 is
Signal A, B : std_logic;
begin

A <= x1 and x2;
 B <= not x2 and x3;
 output <= A or B;

end Behavior;

1.3 Concurrent Assignment Statements

- to assign a value to a signal in an architecture body.
- Four types:
 - Simple signal assignment.
 - Selected signal assignment.
 - Conditional signal assignment.
 - Generate statements.

1.3.1 Simple Signal Assignment

- For a logic or arithmetic expression.
 output <= (x1 and x2) or (not x2 and x3);
- Assign using Others:
 Instead of writing S <= "00000000";
 write S <= (others => '0');

1.3.2 Selected Signal Assignment

- Assign the value of a signal to a **one of several alternatives based on a selection** criterion

```
WITH some_selector SELECT
    output <= x1 WHEN '0',
    <= x2 WHEN OTHERS;
```

1.3.3 Conditional Signal Assignment

- Assign the value of a signal to a **one of several alternatives based on a Condition**

```
output <= '1' WHEN x1 = x2 ELSE
    '0';
```

-- Priority Circuit

-- Libraries to use std_logic

Library IEEE;

Use IEEE.std_logic_1164.all;

-- Entity

Entity priority is

```
    port(x1, x2, x3 :in std_logic;
        output :out std_logic_vector (1 downto 0));  

end priority;
```

-- Architecture

Architecture Behavior of priority is

```

begin

output <= "01" when x1 = '1' else
         "10" when x2 = '1' else
         "11" when x3 = '1' else
         "00" ;

end Behavior;

```

1.3.4 Generate Signal Assignment

- types
 - for generate.
 - if generate.

```

-- Libraries to use std_logic
Library IEEE;
Use IEEE.std_logic_1164.all;

-- Entity
Entity example is
  port(input_signal      :in   std_logic_vector (15 downto 0);
        first_output     :out   std_logic_vector (7  downto 0);
        second_output    :out   std_logic_vector (0  to 7));
end example;

-- Architecture
Architecture Behavior of example is

begin

GENERATE_EXAMPLE : for i in 0 to 7 generate
                    first_output(i) <= input_signal(i);
                    second_output(7 - i) <= input_signal(i + 8);

end generate GENERATE_EXAMPLE;

end Behavior;

-- take a moment and try to understand this code.
-- the code breaks the input to two halves, assign
-- the first half to the first out and
-- the reverse of the second half to the second out
-- input = "1110101100010110"
-- first_output = "00010110"
-- second_output = "11010111"

```

2 Chapter 2

2.1 Components

|

- Intro:
 - VHDL entity defined in one file can be used as a subcircuit in another file.
- The subcircuit is called a component.
- Where is the deceleration?
 - in the declaration region of an architecture.

- Example: Full adder

```
-- Libraries to use std_logic
Library IEEE;
Use IEEE.std_logic_1164.all;

-- Entity
Entity fullAdder1bit is
    port(x, y, carryIn    :in    std_logic;
          sum, carryOut   :out    std_logic);
end fullAdder1bit;

-- Architecture
Architecture Behavior of example is

begin

sum <= x xor y xor carryIn;
carryOut <= (x and y) or (x and carryIn) or (y and carryIn)

end Behavior;
```

- Example: 4 bit Full adder

```
-- Libraries to use std_logic
Library IEEE;
Use IEEE.std_logic_1164.all;

-- Entity
Entity fullAdder4bit is
    port(x, y      :in    std_logic_vector(3 downto 0);
          carryIn  :in    std_logic;
          sum      :out    std_logic_vector(3 downto 0);
          carryOut :out    std_logic);
end fullAdder4bit;

-- Architecture
Architecture Behavior of example is

-- Here we declare an intermediate signal to help us to contain carry of each stage
Signal helpMe : std_logic_vector(1 to 3)

-- Here we declare a component, our 1 bit full adder

Component fullAdder1bit
    port(x, y, carryIn    :in    std_logic;
          sum, carryOut   :out    std_logic);
end Component;

begin

stage0 : fullAdder1bit PORT MAP (carryIn, x(0), y(0), sum(0), helpMe(1));
stage1 : fullAdder1bit PORT MAP (helpMe(1), x(1), y(1), sum(1), helpMe(2));
stage2 : fullAdder1bit PORT MAP (helpMe(2), x(2), y(2), sum(2), helpMe(3));
stage3 : fullAdder1bit PORT MAP (helpMe(3), x(3), y(3), sum(3), carryOut);

-- YOU CAN ALSO TYPE
-- stage3 : fullAdder1bit PORT MAP (x => x(3), y => y(3), carryIn => helpMe(3), sum => sum(3), carry
```

end Behavior;

- Example: 4 bit Full adder (another implementation using for generate)

```
-- Libraries to use std_logic
Library IEEE;
Use IEEE.std_logic_1164.all;

-- Entity
Entity fullAdder4bit is
    port(x, y      :in  std_logic_vector(3 downto 0);
          carryIn  :in  std_logic;
          sum       :out  std_logic_vector(3 downto 0);
          carryOut  :out  std_logic);
end fullAdder4bit;

-- Architecture
Architecture Structure of example is

    -- Here we declare an intermediate signal to help us to contain carry of each stage

    Signal helpMe :  std_logic_vector(0 to 4)

    Component fullAdder1bit
        port(x, y, carryIn      :in  std_logic;
              sum, carryOut     :out  std_logic);
    end Component;

begin

    helpMe(0) <= CarryIn;

    GENERATE_LABEL : for i in 0 to 3 generate
        fullAdder1bit PORT MAP (helpMe(i), x(i), y(i), sum(i), helpMe(i + 1));

    end generate GENERATE_LABEL;
    carryOut <= helpMe(4);
end Structure;
```

- Example: 4 bit Full adder (another implementation)

```
Library IEEE;
Use IEEE.std_logic_1164.all;
Use IEEE.std_logic_signed.all;

Entity fullAdder4bit is
    port(x, y      :in  std_logic_vector(3 downto 0);
          carryIn  :in  std_logic;
          sum       :out  std_logic_vector(3 downto 0);
          carryOut  :out  std_logic);
end fullAdder4bit;

Architecture Behavior of example is

    -- Here we declare an intermediate signal to help us, it will be the summation of x, y and carryIn,
```

```
Signal helpMeSum : std_logic_vector(4 downto 0)
```

```
-- No need to components here!
```

```
begin
```

```
helpMeSum <= ('0' & x) + y + carryIn;
```

```
sum <= helpMeSum(3 downto 0)
```

```
carryOut <= helpMeSum(4)
```

```
end Behavior;
```

- Example: Multiplexers 4to1

```
-- Libraries to use std_logic
```

```
Library IEEE;
```

```
Use IEEE.std_logic_1164.all;
```

```
-- Entity
```

```
Entity mux4to1 is
```

```
    port(w0,w1,w2,w3      :in  std_logic;
```

```
          selector        :in  std_logic_vector(1 downto 0);
```

```
          output          :out  std_logic);
```

```
end mux4to1;
```

```
-- Architecture
```

```
Architecture Behavior of mux4to1 is
```

```
begin
```

```
With selector select
```

```
    output <= w0 when "00",
```


```
          <= w1 when "01",
```

```
          <= w2 when "10",
```

```
          <= w3 when others;
```

```
end Behavior;
```

 - Example: Multiplexers 16to1 using 4to1 mux



```
-- Libraries to use std_logic
```



```

Library IEEE;
Use IEEE.std_logic_1164.all;

-- Entity
Entity mux16to1 is
    port(w          :in    std_logic_vector (0 to 15);
          selector   :in    std_logic_vector(3 downto 0);
          output      :out    std_logic);
end mux16to1;

-- Architecture
Architecture Structure of mux16to1 is

    -- Here we declare an intermediate signal to help us to contain outputs of first 4 muxs as input to

    Signal helpMe :    std_logic_vector(0 to 3)

    -- Here we declare a component, our mux4to1

    Component mux4to1 is
        port(w0,w1,w2,w3      :in    std_logic;
              selector        :in    std_logic_vector(1 downto 0);
              output          :out    std_logic);
    end Component;

begin

    Mux1 : mux4to1 PORT MAP (w(0), w(1), w(2), w(3), selector(1 downto 0), helpMe(0));
    Mux2 : mux4to1 PORT MAP (w(4), w(5), w(6), w(7), selector(1 downto 0), helpMe(1));
    Mux3 : mux4to1 PORT MAP (w(8), w(9), w(10), w(11), selector(1 downto 0), helpMe(2));
    Mux4 : mux4to1 PORT MAP (w(12), w(13), w(14), w(15), selector(1 downto 0), helpMe(3));
    Mux5 : mux4to1 PORT MAP (helpMe(0), helpMe(1), helpMe(2), helpMe(3), selector(3 downto 2), output);
end Structure;

```

- Example 2 to 4 Decoder:

```

Library IEEE;
Use IEEE.std_logic_1164.all;

Entity decoder2to4 is
    port(w          :in    std_logic_vector(1 downto 0);
          Enable     :in    std_logic;
          output      :out    std_logic_vector(0 to 3));
end decoder2to4;

Architecture Behavior of decoder2to4 is

    -- Here we declare an intermediate signal to help us, we concatenate Enable and w with & operator

    Signal Enw :    std_logic_vector(2 downto 0)

begin

    Enw <= Enable & w;
    with Enw select


```

-- 0123

```
output <= "1000" when "100",
         "0100" when "101",
         "0010" when "110",
         "0001" when "111",
         "0000" when others;
```

end Behavior;

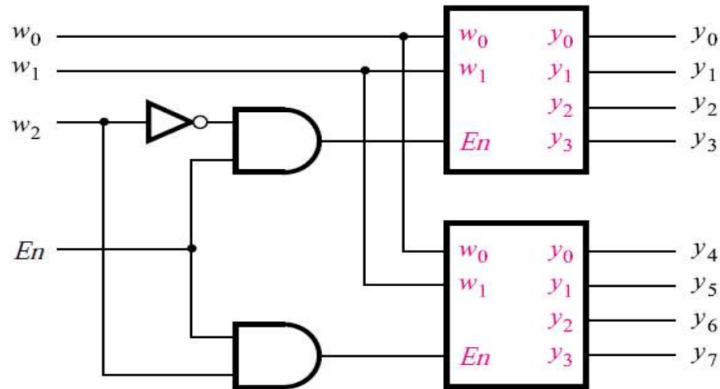- Example: 3 to 8 Decoder using 2 to 4 decoder:



```
Library IEEE;
Use IEEE.std_logic_1164.all;
```

```
Entity decoder3to8 is
    port(w8      :in  std_logic_vector(2 downto 0);
          Enable8 :in  std_logic;
          output8 :out std_logic_vector(0 to 7));
end decoder3to8;
```

Architecture Behavior of decoder3to8 is

-- Here we declare an intermediate signal to help us, we use it as intermediate enable

```
Signal inter_enable : std_logic_vector(0 to 1)
```

-- Here we declare a component, our decoder2to4

```
Component decoder2to4 is
    port(w      :in  std_logic_vector(1 downto 0);
          Enable :in  std_logic;
          output  :out std_logic_vector(0 to 3));
end Component;
```

begin

```
inter_enable(0) <= not w8(2) and Enable8;
inter_enable(1) <= w8(2) and Enable8;
```


```
Stage1 : decoder2to4 PORT MAP (w8(1 downto 0), inter_enable(0), output8(0 to 3) );
```

```

Stage2 : decoder2to4 PORT MAP (w8(1 downto 0), inter_enable(1), output8(4 to 7) );
end Behavior;

```

 - Example: 4 to 1 multiplexer using 2 to 4 decoder:



```

Library IEEE;
Use IEEE.std_logic_1164.all;

```

```

Entity mux4to1 is
    port(w0, w1, w2, w3 :in    std_logic;
          selector      :in    std_logic_vector(1 downto 0);
          output        :out   std_logic);
end mux4to1;

```

Architecture Behavior of mux4to1 is

```

-- Here we declare an intermediate signal to help us, we use it to contain the output of the decoder

```

```

Signal decoder_output : std_logic_vector(0 to 3)

```

```

-- decoder is always enabled

```

```

constant enable : std_logic := '1';

```

```

-- Here we declare a component, our decoder2to4

```

```

Component decoder2to4 is
    port(w          :in    std_logic_vector(1 downto 0);
          Enable    :in    std_logic;
          output     :out   std_logic_vector(0 to 3));
end Component;

```

```

begin

```

```

Stage : decoder2to4 PORT MAP (selector(1 downto 0), enable, decoder_output(0 to 3) );

```

```

with decoder_output select

```

```

    output <= w0 when "1000",

```

```
w1 when "0100",  
w2 when "0010",  
w3 when "0001";
```

```
end Behavior;
```